

Workbook



Table of Contents

Capacitors	2
Capacitors	2


Capacitors

Capacitors


Questions

- 1) A cylindrical capacitor is given. Its length is L , its inner radius is a and its outer radius is b .
 - a. Calculate the capacitance.
 - b. Now two dielectric materials are put in between the plates. k_1 is between a and d , k_2 is from d until b . Calculate the capacitance.
 - c. A dielectric material is inserted between the plates. Its constant is dependent on the radius, $k(r) = k_0 \frac{r}{b}$. Calculate the capacitance in this case.
 - d. We return to the case with the two dielectric materials (from Q2). Calculate the surface area charge distribution.

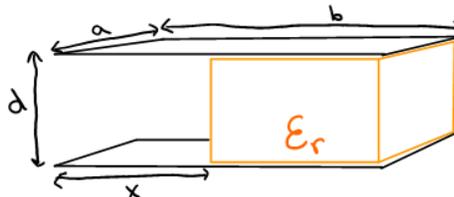
- 2) We are given the following capacitor. The plate length is b , the plate width is a , and the distance between the plates is d . A distance x away from the left edge of the capacitor a dielectric material of constant ϵ_r is inserted.
 - a. Calculate the capacitance of the capacitor.
 - b. A voltage source V_0 is connected. Calculate the charge distribution on capacitor's plates.



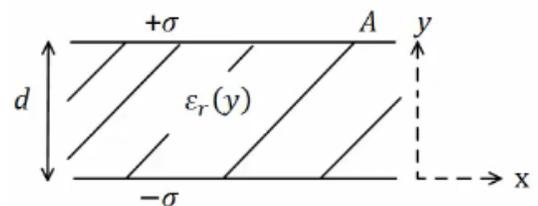
- 3) A parallel plate capacitor is charged with $\pm\sigma$. The area of the plates is A , and the distance between the two plates is d . A dielectric material is placed between the plates. Its dielectric constant is dependent on y and is given by $\epsilon_r(y) = 1 + \left(\frac{y}{d}\right)^2$. The lower plate is located at $y = 0$. Calculate the capacitance.



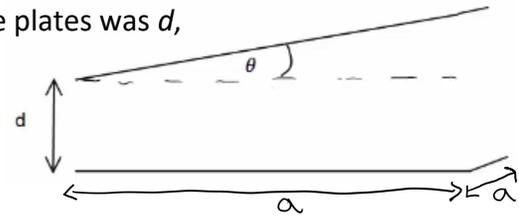
- 4) A parallel plate capacitor was partially deformed at production. Each plate is of length and width a . The distance between the plates was d , but now the upper plate has a deviation of θ , where $\theta \ll \pi$. What is the capacitance of this capacitor as a function of θ ? What is the charge distribution, σ , on the capacitor's plates?



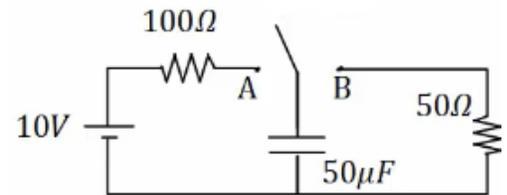
- 5) At $t=0$ the switch is switched to point A. At $t=0.01$ the switch is switched to point B.
- What is the voltage across the capacitor as a function of time?
 - What is the charge on the capacitor at $t=0.02$?
 - What is the current as a function of time?
 - Draw graphs representing the current, and voltage as a function of time.



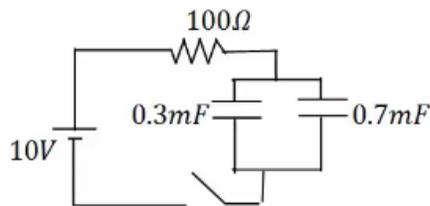
- 6) In the following circuit, at $t=0$, the switch is closed.
- What is the RC time constant for this circuit?
 - Calculate the voltage and charge on each capacitor at times $t=0.2s$ and $t=0.8s$.



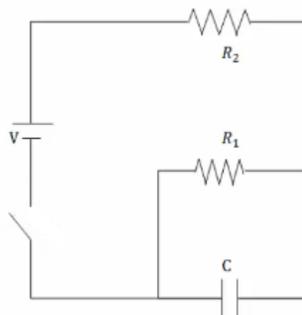
- 7) In the following circuit, at $t=0$, the capacitor has no charge and the switch is closed. Calculate the charge on the capacitor and the current in each resistor as a function of time. We are given V, R_1, R_2, C .



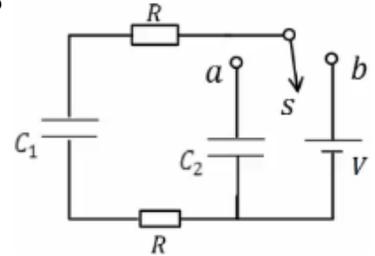
- 8) In the following circuit, capacitor C_1 is charged with charge Q_0 , before the switch is switched to a .
- Write an equation which can be solved to give us the charge on C_1 as a function of time.
 - Solve the equation and calculate the charge on each capacitor as a function of time.
 - What are the currents through each resistor, as a function of time?



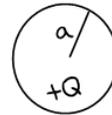- 9) Two spheres of radii a and b are placed far apart, and have charges $+Q$ and $-Q$, respectively.
- Calculate the total electrostatic energy of the system.
 - Using the answer to question 1, calculate the capacitance of the system.
 - If the spheres were to be joined via a very long wire of resistance R , what would be the RC time constant for the discharge of the system?



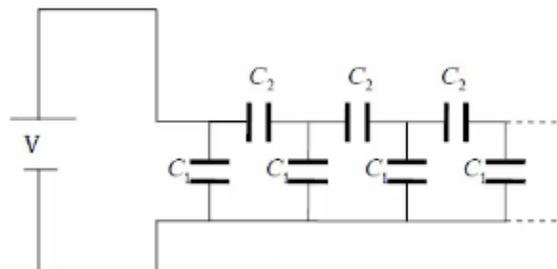- 10) Calculate the total capacitance of the following infinite ladder circuit. Assume that the capacitance of each capacitor is given.



*For the solutions go see the videos